

# Using Laplace Transforms for Circuit Analysis


## First Hour's Agenda

We look at applications of the Laplace Transform for

- Circuit transformation from Time to Complex Frequency
- Complex impedance
- Complex admittance


## Circuit Transformation from Time to Complex Frequency

### Resistive Network - Time Domain

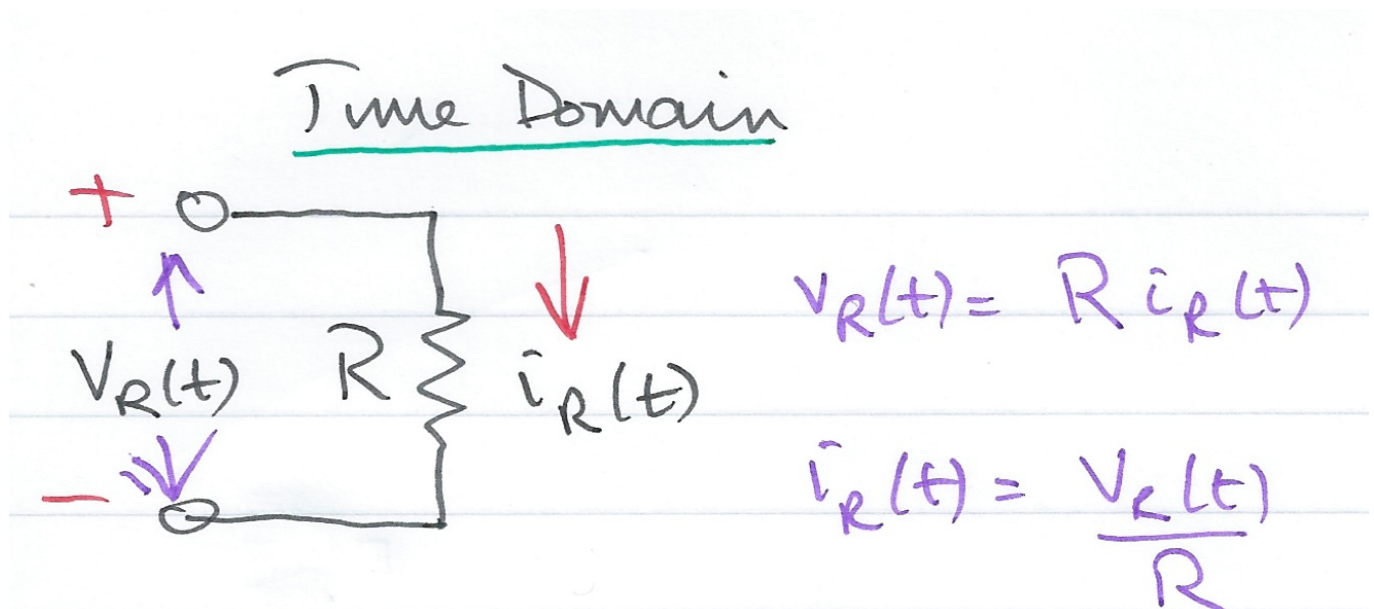

## Resistive Network - Complex Frequency Domain

Frequency Domain

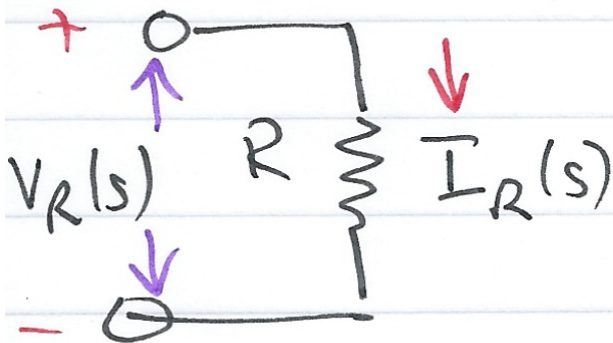


$$V_R(s) = R \bar{I}_R(s)$$

$$\bar{I}_R(s) = \frac{V_R(s)}{R}$$

## Inductive Network - Time Domain

Time Domain

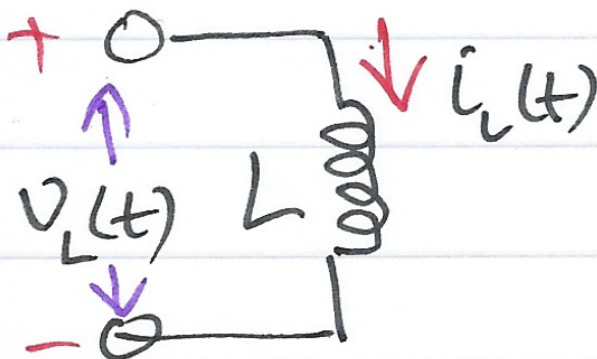


$$V_L(t) = L \frac{di_L}{dt}$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t V_L dt$$

## Inductive Network - Complex Frequency Domain

### Frequency Domain

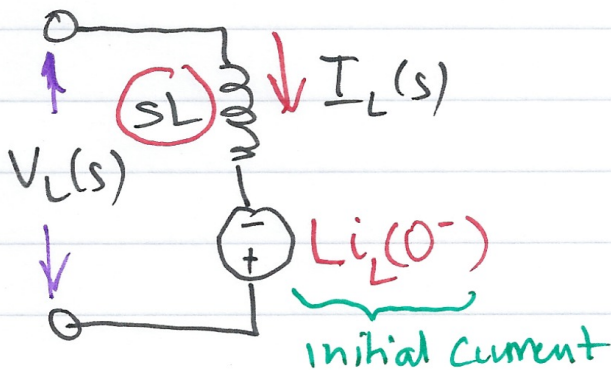


$$V_L(s) = sL I_L(s) - Li_L(0^-)$$

$$I_L(s) = \frac{V_L(s)}{sL} + \frac{i_L(0^-)}{s}$$

## Capacitive Network - Time Domain

### Time Domain

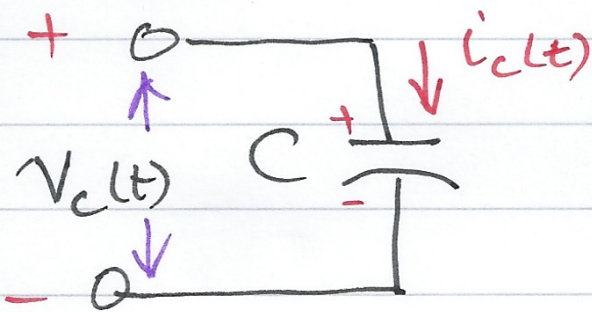


$$i_C(t) = C \frac{dv_C}{dt}$$

$$V_C(t) = \frac{1}{C} \int_{-\infty}^t i_C dt$$

## Capacitive Network - Complex Frequency Domain

### Frequency Domain

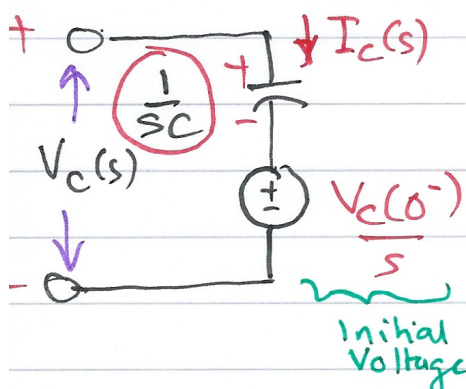

$$I_C(s) = sC V_C(s) - C V_C(0^-)$$


$$V_C(s) = \frac{I_C(s)}{sC} + \frac{V_C(0^-)}{s}$$

## Examples

We will work through these in class. See [worksheet6 \(worksheet6\)](#).
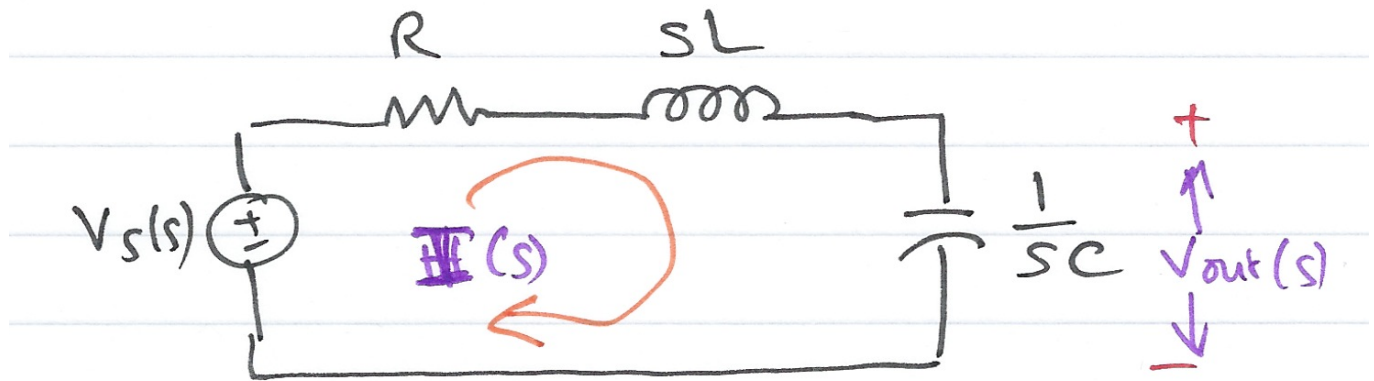
## Complex Impedance $Z(s)$

Consider the  $s$ -domain RLC series circuit, where the initial conditions are assumed to be zero.



For this circuit, the sum

$$R + sL + \frac{1}{sC}$$

represents that total opposition to current flow. Then,

$$I(s) = \frac{V_s(s)}{R + sL + 1/(sC)}$$

and defining the ratio  $V_s(s)/I(s)$  as  $Z(s)$ , we obtain

$$Z(s) = \frac{V_s(s)}{I(s)} = R + sL + \frac{1}{sC}$$

The  $s$ -domain current  $I(s)$  can be found from

$$I(s) = \frac{V_s(s)}{Z(s)}$$


where

$$Z(s) = R + sL + \frac{1}{sC}.$$

Since  $s = \sigma + j\omega$  is a complex number,  $Z(s)$  is also complex and is known as the *complex input impedance* of this RLC series circuit.
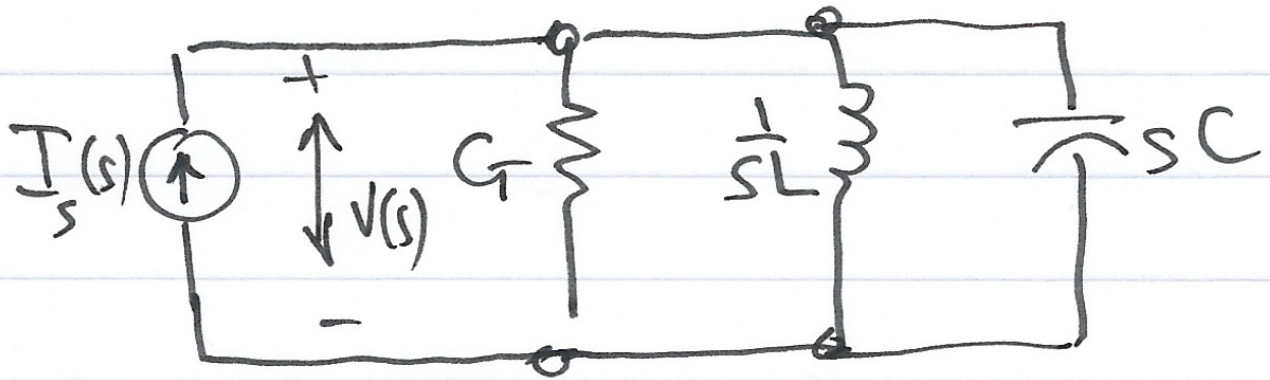
## Complex Admittance $Y(s)$

Consider the  $s$ -domain GLC parallel circuit shown below where the initial conditions are zero.



For this circuit

$$GV(s) + \frac{1}{sL}V(s) + sCV(s) = I_s(s)$$

$$\left(G + \frac{1}{sL} + sC\right)V(s) = I_s(s)$$

Defining the ratio  $I_s(s)/V(s)$  as  $Y(s)$  we obtain

$$Y(s) = \frac{I_s(s)}{V(s)} = G + \frac{1}{sL} + sC = \frac{1}{Z(s)}$$

The  $s$ -domain voltage  $V(s)$  can be found from

$$V(s) = \frac{I_s(s)}{Y(s)}$$

where

$$Y(s) = G + \frac{1}{sL} + sC.$$

$Y(s)$  is complex and is known as the *complex input admittance* of this GLC parallel circuit.