15/02/2019 index

Lab 3: Laplace Transforms and Transfer Functions for Circuit Analysis

Preamble

Associated Class Notes

This lab supports the materials covered in <u>Chapter 3.3 (https://cpjobling.github.io/eg-247-textbook/laplace_transform/3/circuit_analysis)</u> and <u>Chapter 3.4 (https://cpjobling.github.io/eg-247-textbook/laplace_transform/4/transfer_functions)</u> of the course notes. You may wish to refer to the Worksheets <u>worksheet 6 (https://cpjobling.github.io/eg-247-textbook/laplace_transform/3/worksheet6)</u> and <u>worksheet 7 (https://cpjobling.github.io/eg-247-textbook/laplace_transform/4/worksheet7)</u> for additional examples to try.

Other formats

This document is available in <u>HTML (https://cpjobling.github.io/eg-247-textbook/labs/lab03/index)</u> format for online viewing <u>PDF (https://cpjobling.github.io/eg-247-textbook/labs/lab03/lab03.pdf)</u> for printing.

Acknowledgements

These examples have been adapted from Chapter 4 of <u>Stephen Karris</u>, <u>Signals and Systems</u>: <u>With MATLAB Computing and Simulink Modeling (5th Edition) (http://site.ebrary.com/lib/swansea/docDetail.action?</u> <u>docID=10547416</u>).

Tutorial: Defining Transfer Functions in Matlab (not assessed)

The linked m-File is a short tutorial introduction to the definition of transfer functions in Matlab. It introduces the Linear Time Invariant (LTI) block and shows how it can be used in analysis. Download, publish and read the file and use it as a reference for later labs.

Linked m-file: tf matlab.m (tf matlab.m).

Lab Exercise 4

Download the linked script file for the Solution for Example 3 from Week 3. This presents part of the solution to Textbook Example 4.3.

Linked script file solution3.m (solution3.m)

Starting from the simplified circuit (Fig. 4.9 from Karris, 2012: p4-5):

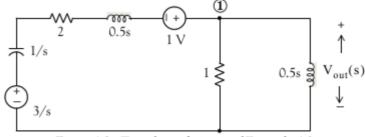


Figure 4.9. Transformed circuit of Example 4.3

15/02/2019 inde

1. Use the Symbolic Toolbox in Matlab to verify

$$V_{out}(s) = \frac{2s(s+3)}{s^3 + 8s^2 + 10s + 4}.$$

2. Use roots to find the factors of the denominator

$$s^3 + 8s^2 + 10s + 4$$

and expand the terms with complex roots to find the quadratic factor.

- 3. Use the inverse Laplace Transform on the rational polynomial with real and quadratic factors to determine the symbolic expression vout as a function of time.
- 4. Verify that the response is

$$v_{out}(t) = \left(1.36e^{-6.57t} + 0.64e^{-0.715t}\cos 0.316t - 1.84e^{-0.715t}\sin 0.316t\right)u_0(t)$$

- 5. Use explot to plot this result.
- 6. Compare your answer with the numerical solution given by the script.

Save your solution as a file with the name ex4.

Lab Exercise 5: Problem Solving in Matlab

Choose one of the Problems Q1-Q3 from Section 4.7 of Karris 2012 (page 4-21) and use MATLAB to adapt the methods used to solve the problem in Lab Exercise 7 to determine the required solution.

Save your chosen solution as a file with the name ex5.

Lab Exercise 6: Complex Impedance and Admittance

The linked file solves Example 4.5 from Karris 2012 (Example 5 in the notes). The solution concerns the calculation of the Complex Impedance and Admittance of the Circuit shown in Figure 4.16.

Linked file: solution5.m (solution5.m).

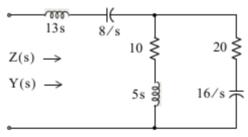


Figure 4.16. Circuit for Example 4.5

Download the file into MATLAB and use it to verify the equation for the circuit impedance Z(s) given in the notes and the text. Extend it to calculate the admittance Y(s).

Use the same technique to solve Q4 from Section 4.7 (Exercises) of Karris (p. 4-21).

Save your solution to a file with the name ex6.

Mini Project 2: Transfer Functions

Download the linked Matlab script which computes the solution to Example 4.7 from Karris (2007) (Example 7 from the notes). This script computes the transfer function of the Op-Amp circuit shown below:

15/02/2019 index

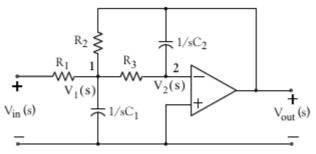


Figure 4.21. The s-domain circuit for Example 4.7

Linked script file: solution7.m (solution7.m)

In the original example:

R1 = 20 kOhm

R2 = 40 kOhm

R3 = 50 kOhm

C1 = 25 nF

C2 = 10 nF

Use your student number to give a different set of component values whiles maintaining the relative sizes.

For example if your number was 876543 you might use:

R1 = 80 kOhm

R2 = 70 kOhm

R3 = 60 kOhm

C1 = 54 nF

C2 = **3**0 nF

If your student number contains 0s, you should substitute a digit if your choice. You may find doc or help and the symbolic toolbox function sym2poly useful.

To Do: save a copy of solution7.m file as proj3. Adapt the script to repeat the computation using component values based on your student number. Then:

- 1. compute and plot the phase response of Gs see function angle
- 2. make a transfer function LTI object Gs2 = tf(numG,denG)
- 3. Compare frequency response with result of bode (Gs2)
- 4. Plot the pole-zero map of Gs2 using the pzmap function.
- 5. Plot the step response of Gs2 using the step function.
- 6. Compute and plot the response of Gs2 to the sinusoid using the lsim function.
- 7. Repeat the simulation of the sinsoidal response in Simulink save model as proj2.slx.

Save your solution as proj2.

What to turn in

15/02/2019 index

You should attach your modified version of the file proj2 along with the Simulink model plus any additional scripts that you wish to claim for to the Lab 3 submission page in OneNote. Complete the claim form and turn-in your assignment through Teams.

You will find it easiest to audit your completion of these exercises by opening the provided *.m files as Live Script files and saving them in this format.

Claim

Up to 3 marks can be claimed for the mini project and up to 2 marks more depending on how much of Exercises 5-6 you have completed.

See <u>Assessment and Feedback: Labwork Assessment (https://docs.google.com/spreadsheets/d/1U-O2hu Th369EHp6mdc1 j 7ARew2WosE93cjsW012c/edit?usp=sharing)</u> for a detailed marking scheme.

The deadline for claims and submission is Midnight, 8th March.