

Homework 4

The Impulse Response and Convolution

The questions for Homework 4 are based on the examples given in [Section 6.8](https://ebookcentral.proquest.com/lib/swansea-ebooks/reader.action?docID=3384197&ppg=207) (<https://ebookcentral.proquest.com/lib/swansea-ebooks/reader.action?docID=3384197&ppg=207>) of {cite karris }.

1. Confirm the result of [Example 5](https://cpjobling.github.io/eg-247-textbook/laplace_transform/5/convolution.html#Example-5) (https://cpjobling.github.io/eg-247-textbook/laplace_transform/5/convolution.html#Example-5) from the notes using the convolution integral

$$h(t) * u_0(t) = \int_{-\infty}^{\infty} u_0(\tau) h(t - \tau) d\tau$$

1. Compute the impulse response $h(t) = i_s(t)$ (where $i_s(t) = \delta(t)$) in terms of R and L for the circuit shown in Fig. Q2 below. Use this result to compute the voltage $v_L(t)$ across the inductor.

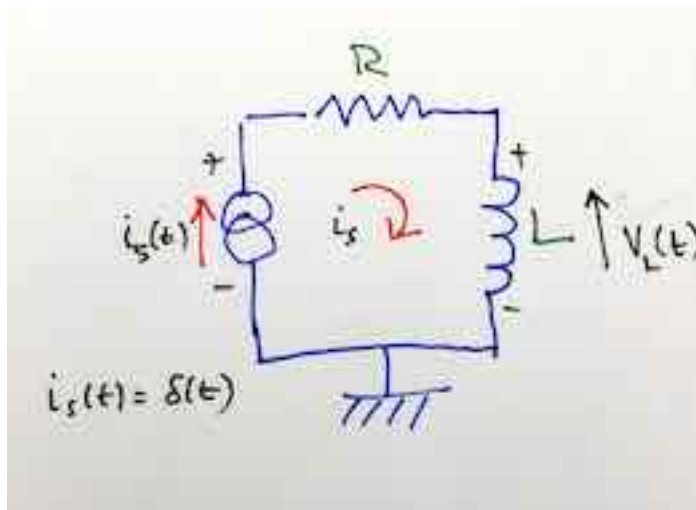


Fig. Q2: An RL Circuit

1. Redo the graphical convolution [Example 2](https://cpjobling.github.io/eg-247-textbook/laplace_transform/5/convolution.html#Example-2) (https://cpjobling.github.io/eg-247-textbook/laplace_transform/5/convolution.html#Example-2) from the notes by forming $h(t - \tau)$ instead of $u(t - \tau)$. That is, use the convolution integral

$$\int_{-\infty}^{\infty} u(\tau) h(t - \tau) d\tau.$$

Confirm the result in MATLAB.

2. Redo the graphical convolution [Example 3 \(https://cpjobling.github.io/eg-247-textbook/laplace_transform/5/convolution.html#Example-3\)](https://cpjobling.github.io/eg-247-textbook/laplace_transform/5/convolution.html#Example-3) from the notes by forming $h(t - \tau)$ instead of $u(t - \tau)$. Confirm the result in MATLAB.
3. Derive the transfer function

$$H(s) = \frac{V_L(s)}{I_s(s)}$$

for the circuit of Fig. Q2.

Use this result to

- a. Confirm the impulse response of this circuit $V_L(t)$.
- b. Compute the step response

$$V_L(t) = \mathcal{L}^{-1} \{ H(s) U_0(s) \} .$$

- c. Validate this result in MATLAB.

4. For the network show in Fig. Q6 compute:

- a. The transfer function

$$H(s) = \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)};$$

- b. The response of this circuit to the input $v_{\text{in}}(t) = u_0(t) - u_0(t - 1)$.
- c. Validate this result in MATLAB.

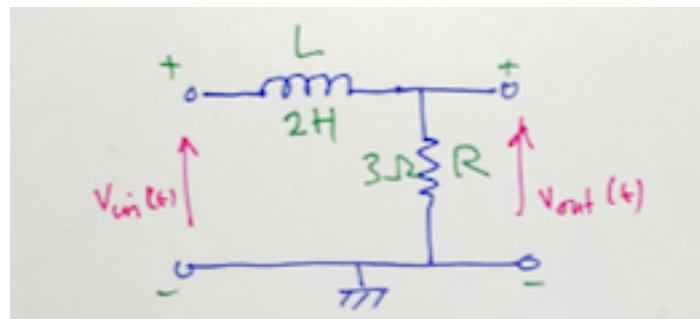


Fig. Q6: An LR Network

5. For the network shown in Fig. Q7 compute:

- a. The transfer function

$$H(s) = \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)};$$

- b. Determine the step response of the network.
- c. State the time constant of the network.
- d. Validate this result in MATLAB.

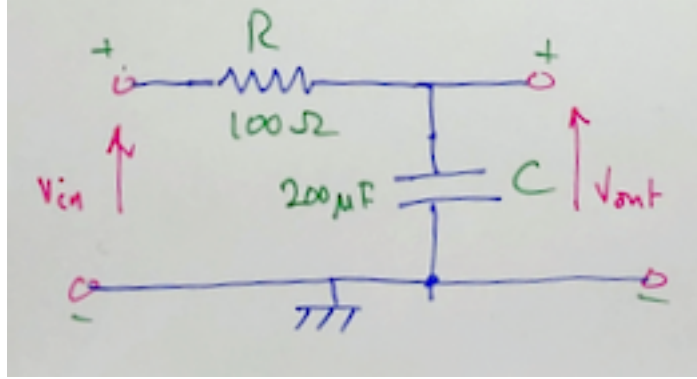


Fig. Q7: An RC Network

Answers to selected problems

- For question 2:

$$h(t) = i_s(t) = \left(\frac{1}{L} \right) e^{-\left(\frac{R}{L}\right)t} u_0(t);$$

$$v_L(t) = - \left(\frac{R}{L} \right) e^{-\left(\frac{R}{L}\right)t} u_0(t) + \delta(t).$$

- For question 5 the transfer function is

$$H(s) = \frac{s}{s + R/L}$$

and the step response is:

$$v_L(t) = L e^{-\left(\frac{R}{L}\right)t} u_0(t).$$

- For question 6 the transfer function is

$$H(s) = \frac{3/2}{s + 3/2}$$

and the pulse response is:

$$v_L(t) = (1 - e^{-1.5t}) u_0(t) - (1 - e^{-1.5(t-1)}) u_0(t - 1).$$

- For question 7 the transfer function is

$$H(s) = \frac{50}{s + 50};$$

the step response is

$$(1 - e^{-50t}) u_0(t)$$

and the time constant is: $T = RC = 1/50$ s.

Reference

{% bibliography --cited %}