

Worksheet 7

To accompany Chapter 3.4 Transfer Functions

We will step through this worksheet in class.

You are expected to have at least watched the video presentation of [Chapter 3.4](https://cpjobling.github.io/eg-247-textbook/laplace_transform/4/transfer_functions) (https://cpjobling.github.io/eg-247-textbook/laplace_transform/4/transfer_functions) of the [notes](https://cpjobling.github.io/eg-247-textbook) (<https://cpjobling.github.io/eg-247-textbook>) before coming to class. If you haven't watch it afterwards!

Second Hour's Agenda

- Transfer Functions
- A Couple of Examples
- Circuit Analysis Using MATLAB LTI Transfer Function Block
- Circuit Simulation Using Simulink Transfer Function Block


In []:

```
% Matlab setup  
clear all  
format compact
```

Transfer Functions for Circuits

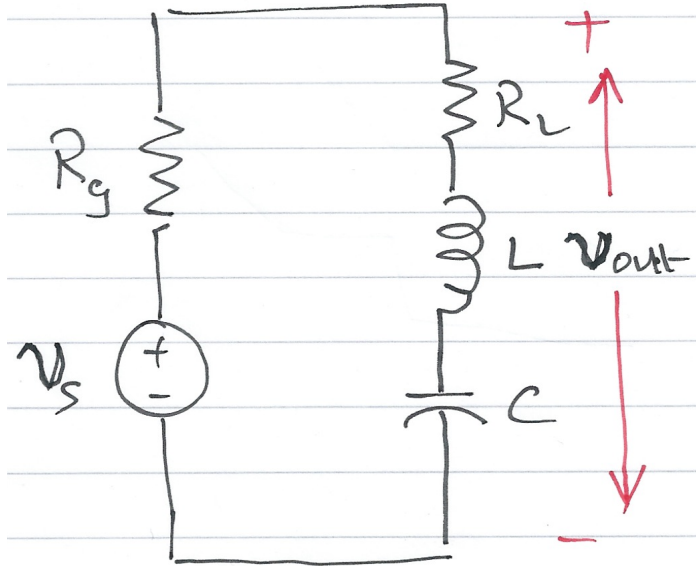Example 6

Derive an expression for the transfer function $G(s)$ for the circuit below. In this circuit R_g represents the internal resistance of the applied (voltage) source v_s , and R_L represents the resistance of the load that consists of R_L , L and C .



Sketch of Solution

- Replace $v_s(t)$, R_g , R_L , L and C by their transformed (*complex frequency*) equivalents: $V_s(s)$, R_g , R_L , sL and $1/(sC)$
- Use the *Voltage Divider Rule* to determine $V_{\text{out}}(s)$ as a function of $V_s(s)$
- Form $G(s)$ by writing down the ratio $V_{\text{out}}(s)/V_s(s)$

Worked solution.

Pencast: [ex6.pdf \(../worked_examples/ex6.pdf\)](#) - open in Adobe Acrobat Reader.

Answer


$$G(s) = \frac{V_{\text{out}}(s)}{V_s(s)} = \frac{R_L + sL + 1/sC}{R_g + R_L + sL + 1/sC}.$$

Example 7

Compute the transfer function for the op-amp circuit shown below in terms of the circuit constants R_1 , R_2 , R_3 , C_1 and C_2 . Then replace the complex variable s with $j\omega$, and the circuit constants with their numerical values and plot the magnitude

$$|G(j\omega)| = \frac{|V_{\text{out}}(j\omega)|}{|V_{\text{in}}(j\omega)|}$$

versus radian frequency ω rad/s.

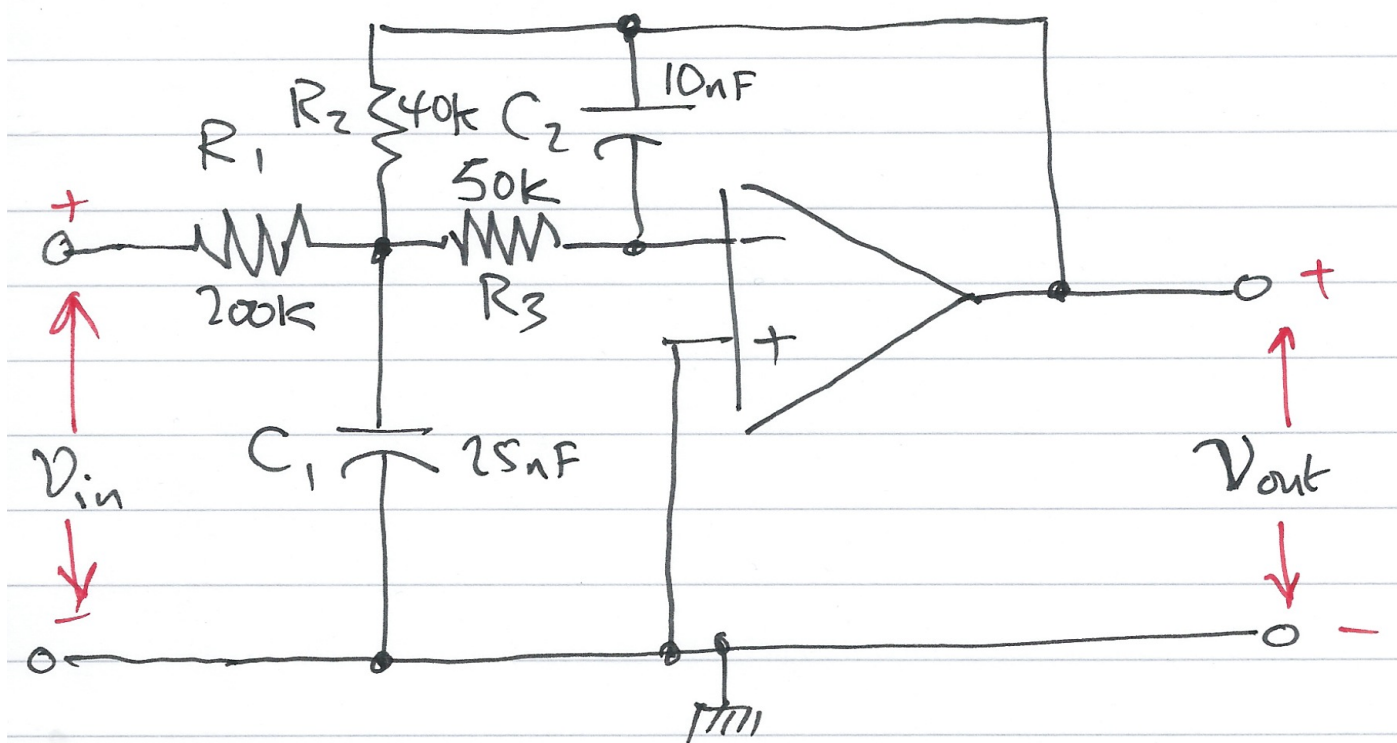

Sketch of Solution

- Replace the components and voltages in the circuit diagram with their complex frequency equivalents
- Use nodal analysis to determine the voltages at the nodes either side of the 50K resistor R_3
- Note that the voltage at the input to the op-amp is a virtual ground
- Solve for $V_{\text{out}}(s)$ as a function of $V_{\text{in}}(s)$
- Form the reciprocal $G(s) = V_{\text{out}}(s)/V_{\text{in}}(s)$
- Use MATLAB to calculate the component values, then replace s by $j\omega$.
- Plot

$$|G(j\omega)|$$

on log-linear "paper".

Worked solution.

Pencast: [ex7.pdf \(../worked_examples/ex7.pdf\)](#) - open in Adobe Acrobat Reader.

Answer

$$G(s) = \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)} = \frac{-1}{R_1 ((1/R_1 + 1/R_2 + 1/R_3 + sC_1)(sC_2R_3) + 1/R_2)}.$$

The Matlab Bit

See attached script: [solution7.m \(../matlab/solution7.m\)](#).

Week 3: Solution 7

In []:

```
syms s;
```

In []:

```
R1 = 200*10^3;  
R2 = 40*10^3;  
R3 = 50*10^3;  
  
C1 = 25*10^(-9);  
C2 = 10*10^(-9);
```

In []:

```
den = R1*((1/R1+ 1/R2 + 1/R3 + s*C1)*(s*R3*C2) + 1/R2);  
simplify(den)
```

Result is: $100*s*((7555786372591433*s)/302231454903657293676544 + 1/20000) + 5$

Simplify coefficients of s in denominator

In []:

```
format long  
denG = sym2poly(ans)
```

In []:

```
numG = -1;
```

Plot

For convenience, define coefficients a and b :

In []:

```
a = denG(1);  
b = denG(2);
```

In []:

```
w = 1:10:10000;
```

$$G(j\omega) = \frac{-1}{a\omega^2 - jb\omega + 5}$$

In []:

```
Gs = -1./ (a*w.^2 - j.*b.*w + denG(3));
```


In []:

```
semilogx(w, abs(Gs))  
xlabel('Radian frequency w (rad/s')  
ylabel('|Vout/Vin|')  
title('Magnitude Vout/Vin vs. Radian Frequency')  
grid
```

Using Transfer Functions in Matlab for System Analysis

Please use the file [tf_matlab.m \(../matlab/tf_matlab.m\)](#) to explore the Transfer Function features provide by Matlab. Use the *publish* option to generate a nicely formatted document.

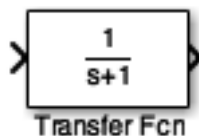Using Transfer Functions in Simulink for System Simulation



The Simulink transfer function (**Transfer Fcn**) block shown above implements a transfer function representing a general input output function

$$G(s) = \frac{N(s)}{D(s)}$$

that it is not specific nor restricted to circuit analysis. It can, however be used in modelling and simulation studies.

Example

Recast Example 7 as a MATLAB problem using the LTI Transfer Function block.

For simplicity use parameters $R_1 = R_2 = R_3 = 1 \Omega$, and $C_1 = C_2 = 1 \text{ F}$.

Calculate the step response using the LTI functions.

Verify the result with Simulink.

The Matlab solution: [example8.m \(../matlab/example8.m\)](#).

MATLAB Solution

From a previous analysis the transfer function is:

$$G(s) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{-1}{R_1 [(1/R_1 + 1/R_2 + 1/R_3 + sC_1)(sR_3 C_2) + 1/R_2]}$$

so substituting the component values we get:

$$G(s) = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{-1}{s^2 + 3s + 1}$$

We can find the step response by letting $v_{\text{in}}(t) = u_0(t)$ so that $V_{\text{in}}(s) = 1/s$ then

$$V_{\text{out}}(s) = \frac{-1}{s^2 + 3s + 1} \cdot \frac{1}{s}$$

We can solve this by partial fraction expansion and inverse Laplace transform as is done in the text book with the help of Matlab's `residue` function.

Here, however we'll use the LTI block that was introduced in the lecture.

Define the circuit as a transfer function

In []:

```
G = tf([-1],[1 3 1])
```

step response is then:

In []:

```
step(G)
```

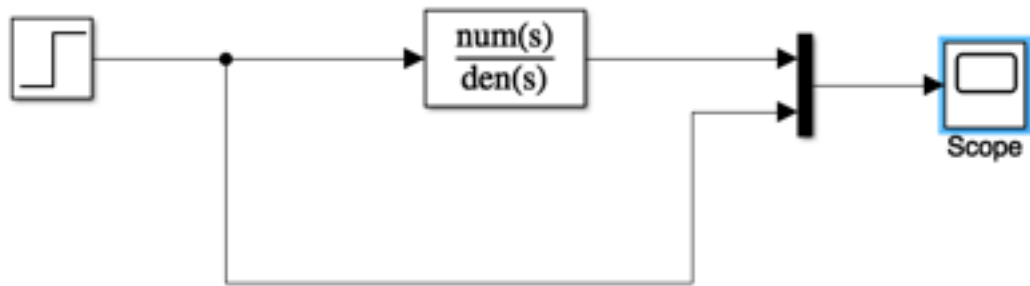

Simples!

Simulink model


See [example_8.slx](#) ([../matlab/example_8.slx](#)).

In []:

```
open example_8
```



Result

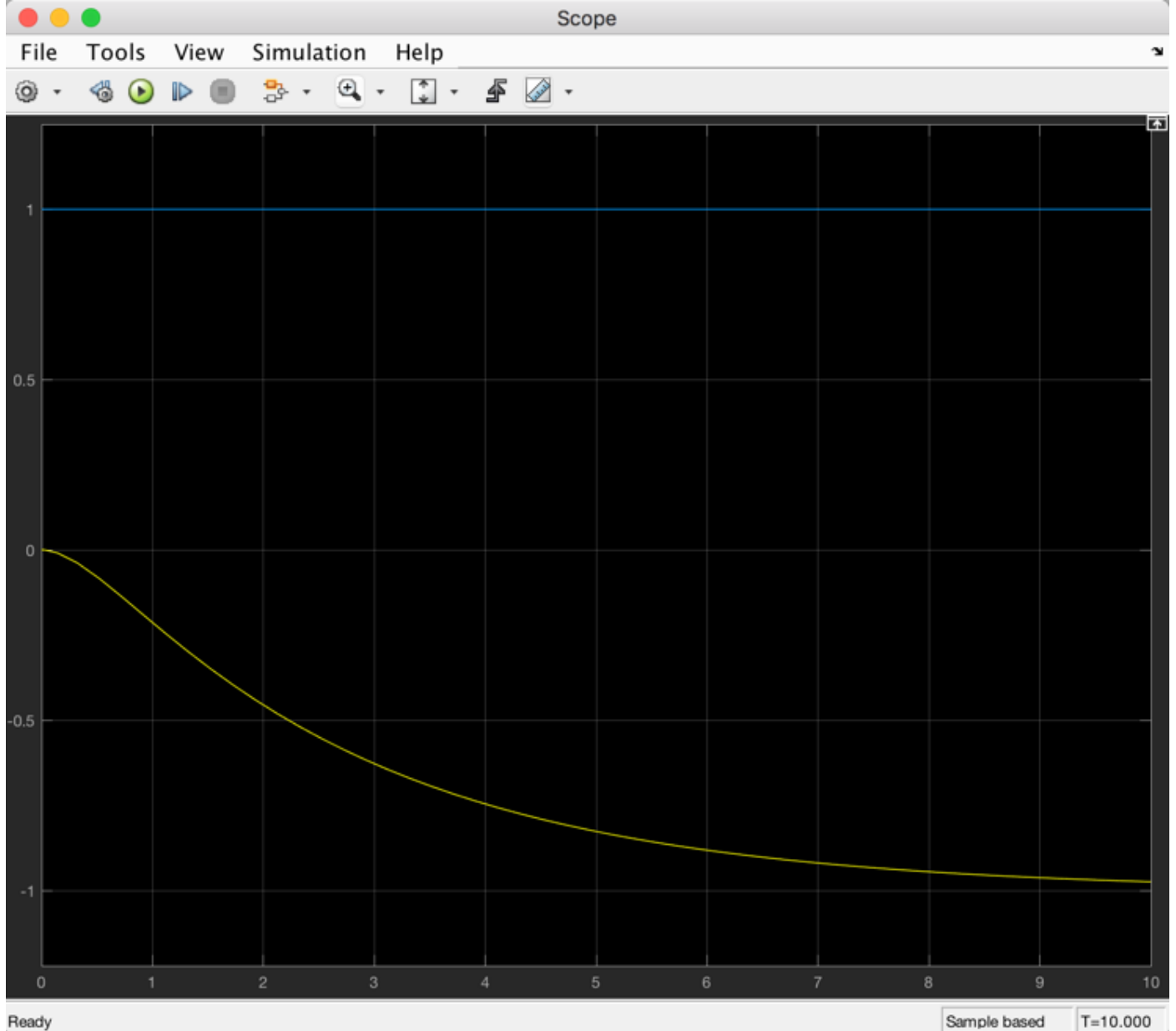

Let's go a bit further by finding the frequency response:

In []:

```
bode(G)
```

Matlab Solutions

For convenience, single script MATLAB solutions to the examples are provided and can be downloaded from the accompanying [MATLAB \(../matlab\)](#) folder.

- Solution 7 [[solution7.m \(../matlab/solution7.m\)](#)]
- Example 8 [[example8.m \(../matlab/example8.m\)](#)]
- Simulink model [[example8.slx \(../matlab/example8.slx\)](#)]

In []:

```
cd ../matlab  
ls  
open solution7
```