Lecturer: Set up MATLAB


In [44]:

format compact
clear all

Elementary Signals

An annotatable copy of partial notes and in-class examples for this presentation will be distributed before the first class meeting as **Worksheet 3** the handouts section of the _Content Library of the **OneNote Class Notebook** for this class. You can also view the notes for this presentation as a webpage (https://cpjobling.github.io/cpjobling/eg-247-textbook/elementary_signals/index)) and as a downloadable https://cpjobling.github.io/cpjobling.github.io/cpjobling/eg-247-textbook/elementary_signals/elementary_signals.pdf).

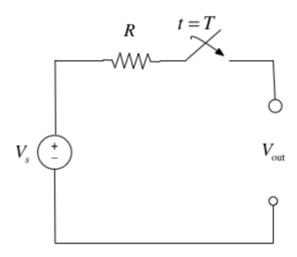Consider the network shown below, where the switch is closed at time t = T.



Express the output voltage v_{out} as a function of the unit step function, and sketch the appropriate waveform.

Solution


Before the switch is closed at t < T,

$$V_{\rm out} = 0.$$

After the switch is closed for t > T,

$$V_{\rm out} = V_s$$
.

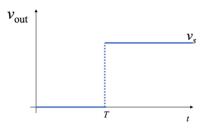
We imagine that the voltage jumps instantaneously from 0 to V_s volts at t=T seconds.



We call this type of signal a step function.

The Unit Step Function
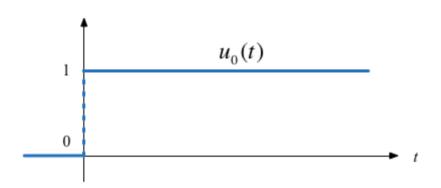
$$u_0(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$



In Matlab

In Matlab, we use the heaviside function (Named after Oliver Heaviside (http://en.wikipedia.org/wiki/Oliver Heaviside)).

In [15]:


```
%%file plot_heaviside.m

syms t
ezplot(heaviside(t),[-1,1])
heaviside(0)
```

Created file '/Users/eechris/dev/eg-247/content/elementary_signals/s how_heaviside.m'.

In [16]:

plot_heaviside

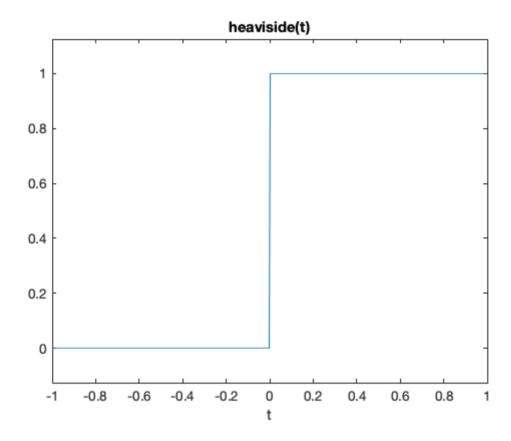

Note that, so that it can be plotted, Matlab defines the *heaviside function* slightly differently from the mathematically ideal unit step:

heaviside(t) =
$$\begin{cases} 0 & t < 0 \\ 1/2 & t = 0 \\ 1 & t > 0 \end{cases}$$


Simple Signal Operations

Amplitude Scaling

Sketch $Au_0(t)$ and $-Au_0(t)$


In [25]:
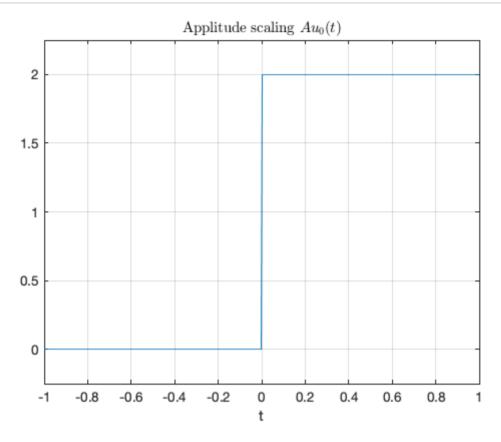
```
syms t;
u0(t) = heaviside(t); % rename heaviside function for ease of use
A = 2; % so signal can be plotted
ezplot(A*u0(t),[-1,1]),grid,title('Applitude scaling $$Au_0(t)$$','interpreter','latex')
```



Note that the signal is scaled in the y direction.

In [26]:

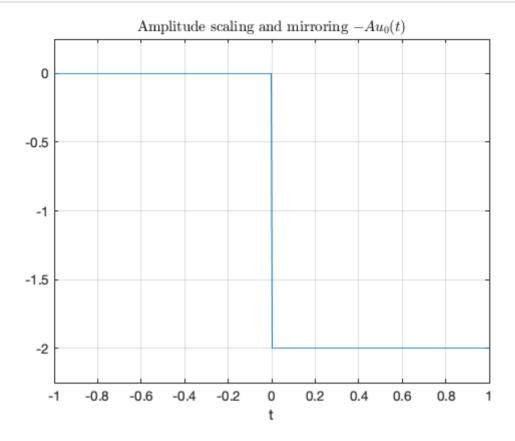


Note that, because of the sign, the signal is mirrored about the x axis as well as being scaled by 2.

Time Reversal

Sketch $u_0(-t)$

In [23]:

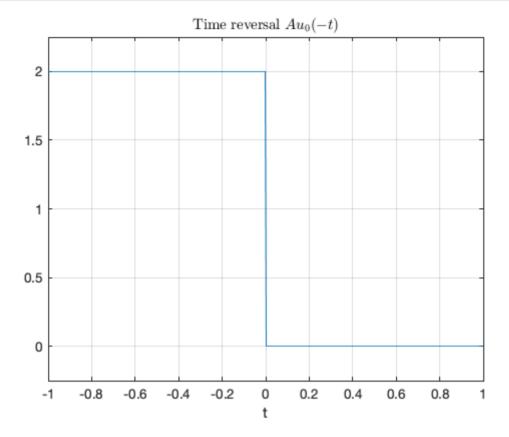 $ezplot(A*u0(-t),[-1,1]),grid,title('Time reversal <math>Au_0(-t)$,'interpreter','latex')




The sign on the function argument -t causes the whole signal to be reversed in time. Note that another way of looking at this is that the signal is mirrored about the y axis.

Time Delay and Advance

Sketch $u_0(t-T)$ and $u_0(t+T)$

In [22]:

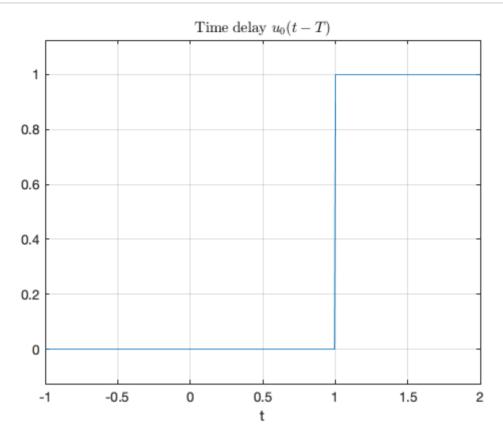
T = 1; % again to make the signal plottable. ezplot(u0(t - T),[-1,2]),grid,title('Time delay $\u_0(t - T),\u_1(t - T),\u_1(t$



This is a *time delay* ... note for $u_0(t-T)$ the step change occurs T seconds **later** than it does for $u_0(t)$.

In [28]:

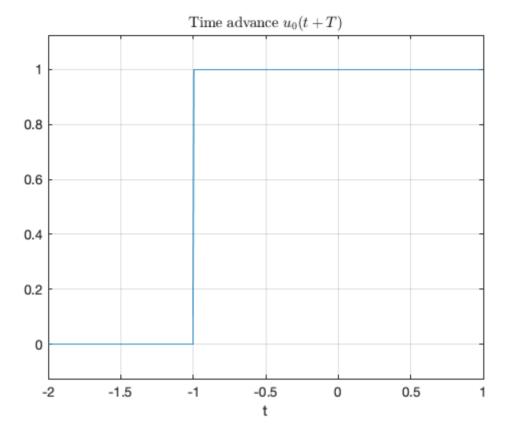ezplot(u0(t + T),[-2,1]),grid,title('Time advance $\u_0(t + T)$,'interpreter', 'latex')



This is a *time advance* ... note for $u_0(t+T)$ the step change occurs T seconds **earlier** than it does for $u_0(t)$.


Examples

We will work through some examples in class. See Worksheet 3 (worksheet3).

Synthesis of Signals from the Unit Step

Unit step functions can be used to represent other time-varying functions such as rectangular pulses, square waves and triangular pulses. See <u>Worksheet 3 (worksheet3)</u> for the examples that we will look at in class.

The Ramp Function

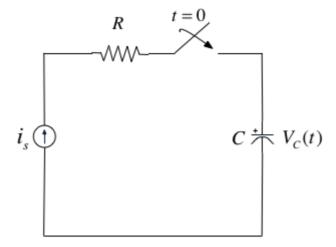

In the circuit shown above $i_{\scriptscriptstyle S}$ is a constant current source and the switch is closed at time t=0.


The voltage across the capacitor can be represented as

$$v_C(t) = \frac{i_s}{C} t u_0(t)$$

To sketch the wave form, let's arbitrarily let C and $i_{\it s}$ be one and then plot with MATLAB.

```
In [32]:
```
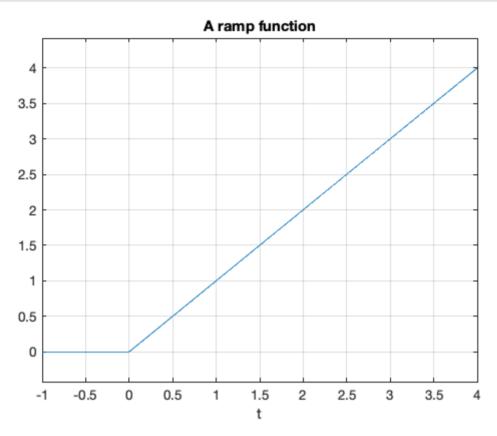
```
C = 1; is = 1;
vc(t)=t*u0(t);
ezplot(vc(t),[-1,4]),grid,title('A ramp function')
```



This type of signal is called a **ramp function**. Note that it is the *integral* of the step function (the resistor-capacitor circuit implements a simple integrator circuit).

The unit ramp function is defined as

 $u_1(t) = \int_{-\infty}^{t} u_0(\tau) d\tau$

so

$$u_1(t) = \begin{cases} 0 & t < 0 \\ t & t \ge 0 \end{cases}$$

and

$$u_0(t) = \frac{d}{dt}u_1(t)$$

Note


Higher order functions of *t* can be generated by the repeated integration of the unit step function.

For future reference, you should determine $u_2(t)$, $u_3(t)$ and $u_n(t)$ for yourself and make a note of the general rule:

$$u_{n-1} = \frac{1}{n} \frac{d}{dt} u_n(t)$$

Details are given in equations 1.26—1.29 in Karris.

The Dirac Delta Function

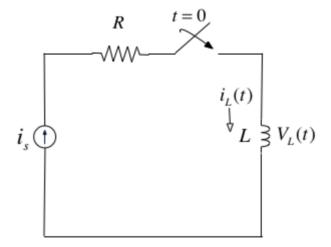

In the circuit shown above, the switch is closed at time t=0 and $i_L(t)=0$ for t<0. Express the inductor current $i_L(t)$ in terms of the unit step function and hence derive an expression for $v_L(t)$.

Solution

$$v_L(t) = L \frac{di_L}{dt}$$

Because the switch closes instantaneously at t = 0

$$i_L(t) = i_s u_0(t)$$

Thus

$$v_L(t) = i_s L \frac{d}{dt} u_0(t).$$

To solve this problem we need to invent a function that represents the derivative of the unit step function. This function is called $\delta(t)$ or the *dirac delta* function (named after <u>Paul Dirac</u>). (http://en.wikipedia.org/wiki/Paul Dirac)).

The delta function

The unit impulse or the delta function, denoted as $\delta(t)$, is the derivative of the unit step.

This function is tricky because $u_0(t)$ is discontinuous at t=0 but it must have the properties

$$\int_{-\infty}^{t} \delta(\tau)d\tau = u_0(t)$$

and

$$\delta(t) = 0 \ \forall \ t \neq 0.$$

Sketch of the delta function



MATLAB Confirmation

In [43]:

```
is = 1; L = 1;
vL(t) = is * L * diff(u0(t))
```

vL(t) =

dirac(t)

Note that we can't plot dirac(t) in MATLAB with ezplot.

Important properties of the delta function

Sampling Property

The sampling property of the delta function states that

$$f(t)\delta(t-a) = f(a)\delta(t-a)$$

or, when a = 0,

$$f(t)\delta(t) = f(0)\delta(t)$$

Multiplication of any function f(t) by the delta function $\delta(t)$ results in sampling the function at the time instants for which the delta function is not zero.

The study of descrete-time (sampled) systems is based on this property.

You should work through the proof for youself.

Sifting Property

The sifting property of the delta function states that

$$\int_{-\infty}^{\infty} f(t)\delta(t-\alpha)dt = f(\alpha)$$

That is, if multiply any function f(t) by $\delta(t-\alpha)$, and integrate from $-\infty$ to $+\infty$, we will get the value of f(t) evaluated at $t=\alpha$.

You should also work through the proof for yourself.

Higher Order Delta Fuctions

the nth-order delta function is defined as the nth derivative of $u_0(t)$, that is

$$\delta^n(t) = \frac{d^n}{dt^n} [u_0(t)]$$

The function $\delta'(t)$ is called the *doublet*, $\delta''(t)$ is called the *triplet* and so on.

By a procedure similar to the derivation of the sampling property we can show that

$$f(t)\delta'(t-a) = f(a)\delta'(t-a) - f'(t)\delta(t-a)$$

Also, derivation of the sifting property can be extended to show that

$$\int_{-\infty}^{\infty} f(t)\delta^{n}(t-\alpha)dt = (-1)^{n} \frac{d^{n}}{dt^{n}} [f(t)] \Big|_{t=\alpha}$$

Summary

In this chapter we have looked at some elementary signals and the theoretical circuits that can be used to generate them.

Takeaways

- You should note that the unit step is the *heaviside function* $u_0(t)$.
- Many useful signals can be synthesized by use of the unit step as a "gating function" in combination with other signals
- That unit ramp function $u_1(t)$ is the integral of the step function.
- The *Dirac delta* function $\delta(t)$ is the derivative of the unit step function. We sometimes refer to it as the *unit impulse function*.
- The delta function has sampling and sifting properties that will be useful in the development of *time* convolution and sampling theory. and that

Examples

We will do some of these in class. See worksheet3 (worksheet3).

Homework

These are for you to do later for further practice. See Homework 1 (hw1).