

Lecturer: Clear all the cells and set up MATLAB

In [1]:

```
format compact
clear all
```

## Elementary Signals


The preparatory reading for this section is Chapter 1 of Karris

(<https://ebookcentral.proquest.com/lib/swansea-ebooks/reader.action?docID=3384197&ppg=75#ppg=17>), which

- begins with a discussion of the elementary signals that may be applied to electrical circuits
- introduces the unit step, unit ramp and dirac delta functions
- presents the sampling and sifting properties of the delta function and
- concludes with examples of how other useful signals can be synthesised from these elementary signals.

An annotatable copy of partial notes and in-class examples for this presentation will be distributed before the first class meeting as **Worksheet 3** the handouts section for week 1 of the *\_Content Library* of the **OneNote Class Notebook**. You can also view the notes for this presentation as a webpage ([HTML](https://cpjobling.github.io/eg-247-textbook/elementary_signals/index.html) ([https://cpjobling.github.io/eg-247-textbook/elementary\\_signals/index.html](https://cpjobling.github.io/eg-247-textbook/elementary_signals/index.html))) and as a downloadable [PDF file](https://cpjobling.github.io/cpjobling/eg-247-textbook/elementary_signals/elementary_signals.pdf) ([https://cpjobling.github.io/cpjobling/eg-247-textbook/elementary\\_signals/elementary\\_signals.pdf](https://cpjobling.github.io/cpjobling/eg-247-textbook/elementary_signals/elementary_signals.pdf)).

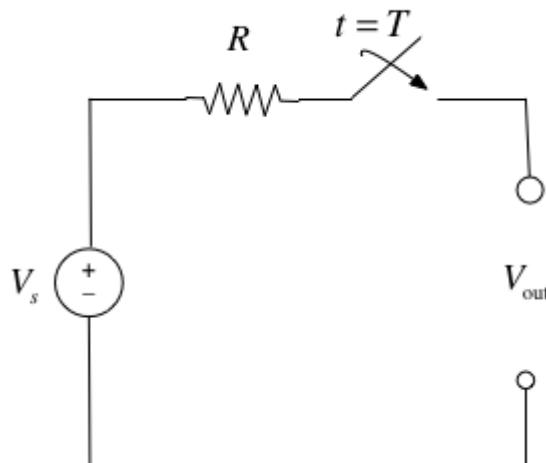Consider the network shown below, where the switch is closed at time  $t = T$ .



Express the output voltage  $v_{out}$  as a function of the unit step function, and sketch the appropriate waveform.

## Solution


Before the switch is closed at  $t < T$ ,

$$V_{\text{out}} = 0.$$

After the switch is closed for  $t > T$ ,

$$V_{\text{out}} = V_s.$$

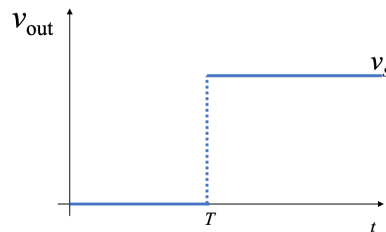
We imagine that the voltage jumps instantaneously from 0 to  $V_s$  volts at  $t = T$  seconds.



We call this type of signal a step function.
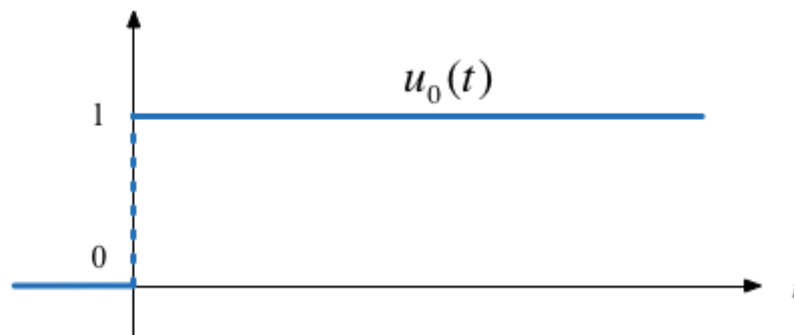
## The Unit Step Function

$$u_0(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$



## In Matlab

In Matlab, we use the `heaviside` function (Named after [Oliver Heaviside](http://en.wikipedia.org/wiki/Oliver_Heaviside) ([http://en.wikipedia.org/wiki/Oliver\\_Heaviside](http://en.wikipedia.org/wiki/Oliver_Heaviside))).

In [2]:


```
%%file plot_heaviside.m
syms t
ezplot(heaviside(t),[-1,1])
heaviside(0)
```

Created file '/Users/eechris/dev/eg-247-textbook/content/elementary\_signals/plot\_heaviside.m'.

In [3]:

```
plot_heaviside
```

```
ans =  
0.5000
```

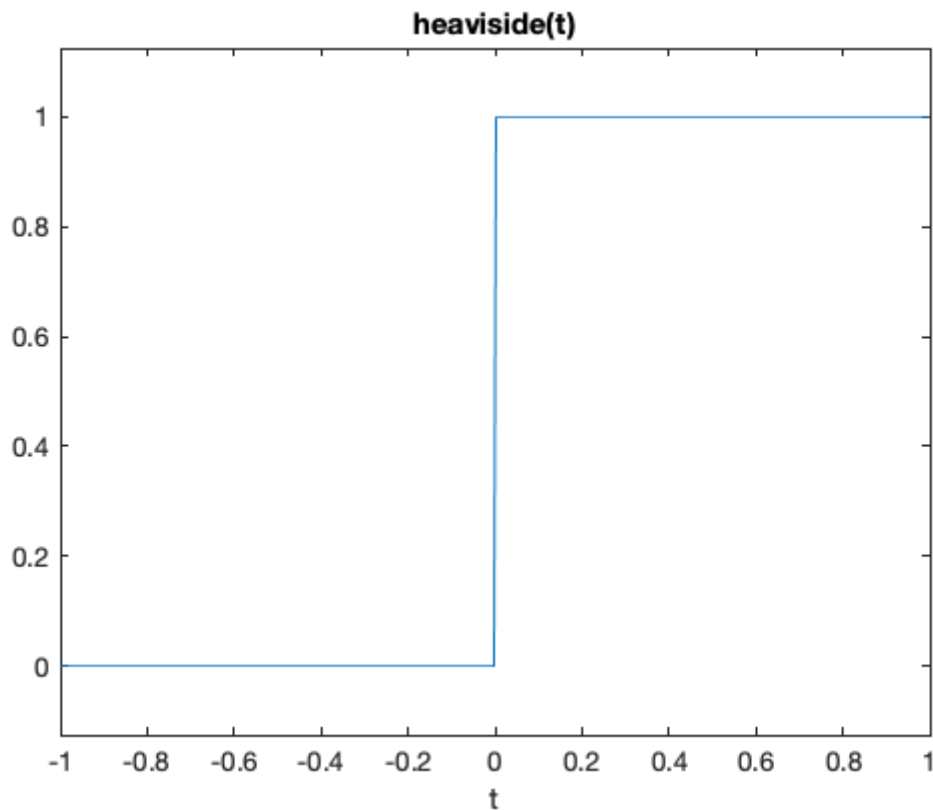

Note that, so that it can be plotted, Matlab defines the *heaviside function* slightly differently from the mathematically ideal unit step:

$$\text{heaviside}(t) = \begin{cases} 0 & t < 0 \\ 1/2 & t = 0 \\ 1 & t > 0 \end{cases}$$


## Simple Signal Operations

### Amplitude Scaling

Sketch  $Au_0(t)$  and  $-Au_0(t)$

In [4]:

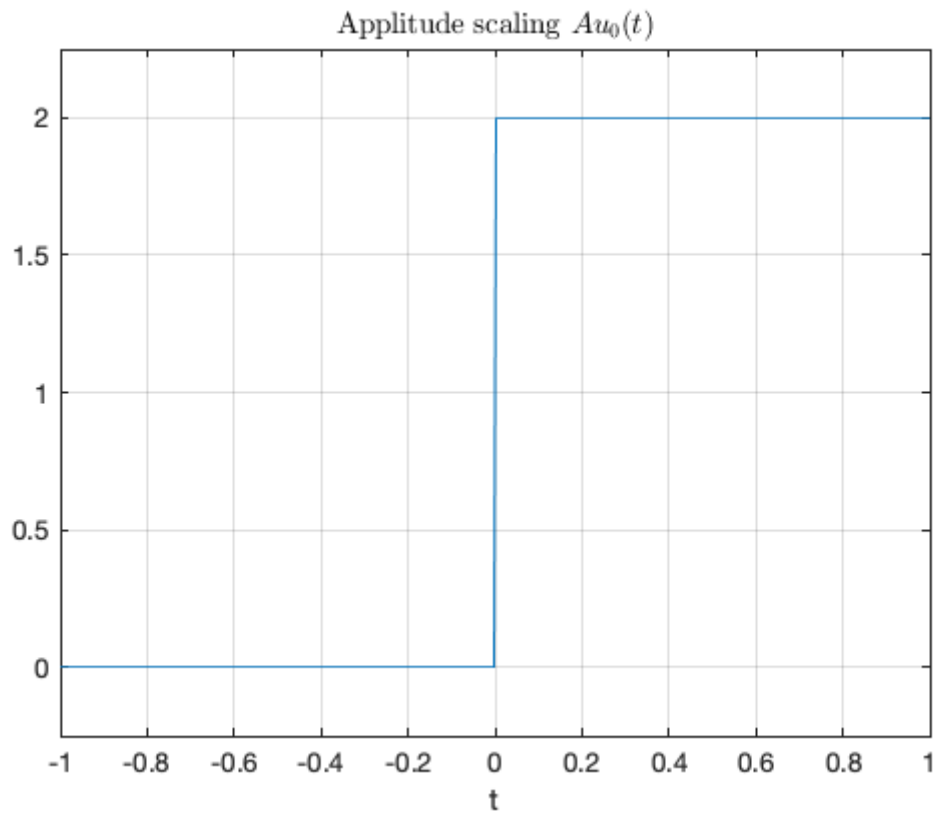
```
syms t;  
u0(t) = heaviside(t); % rename heaviside function for ease of use  
A = 2; % so signal can be plotted  
ezplot(A*u0(t),[-1,1]),grid,title('Applitude scaling  $Au_0(t)$ ','interpreter',  
'latex')
```



Note that the signal is scaled in the y direction.

In [5]:
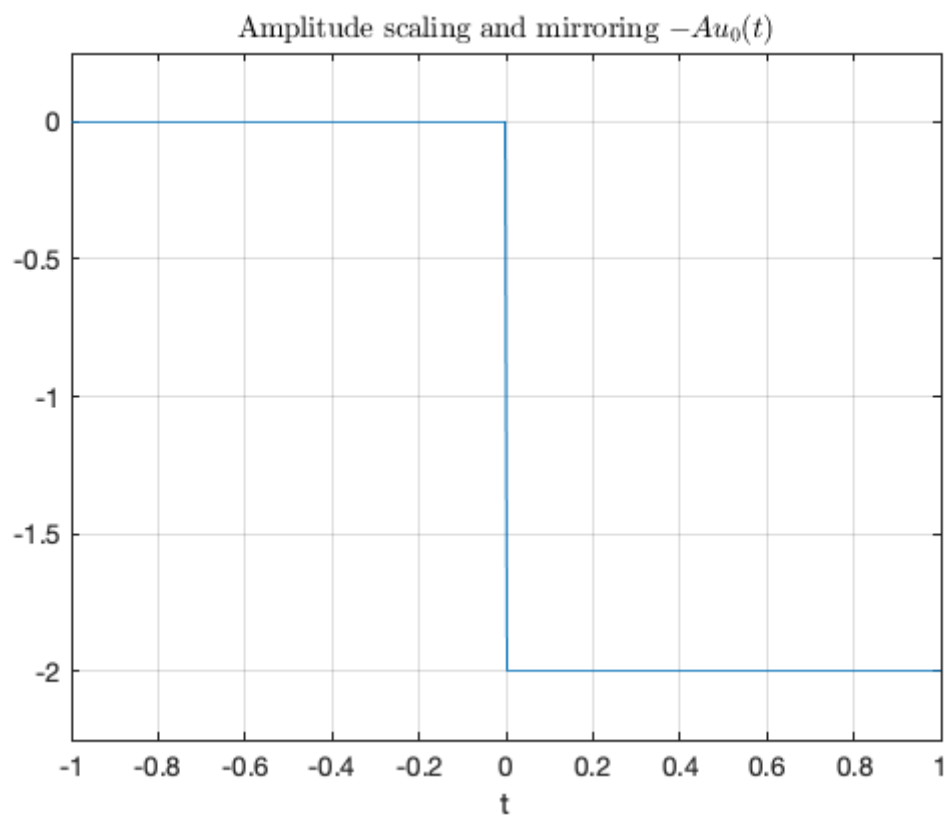
```
ezplot(-A*u0(t),[-1,1]),grid,title('Amplitude scaling and mirroring  $-Au_0(t)$ '),  
      'interpreter','latex')
```




Note that, because of the sign, the signal is mirrored about the  $x$  axis as well as being scaled by 2.

## Time Reversal

Sketch  $u_0(-t)$

In [6]:
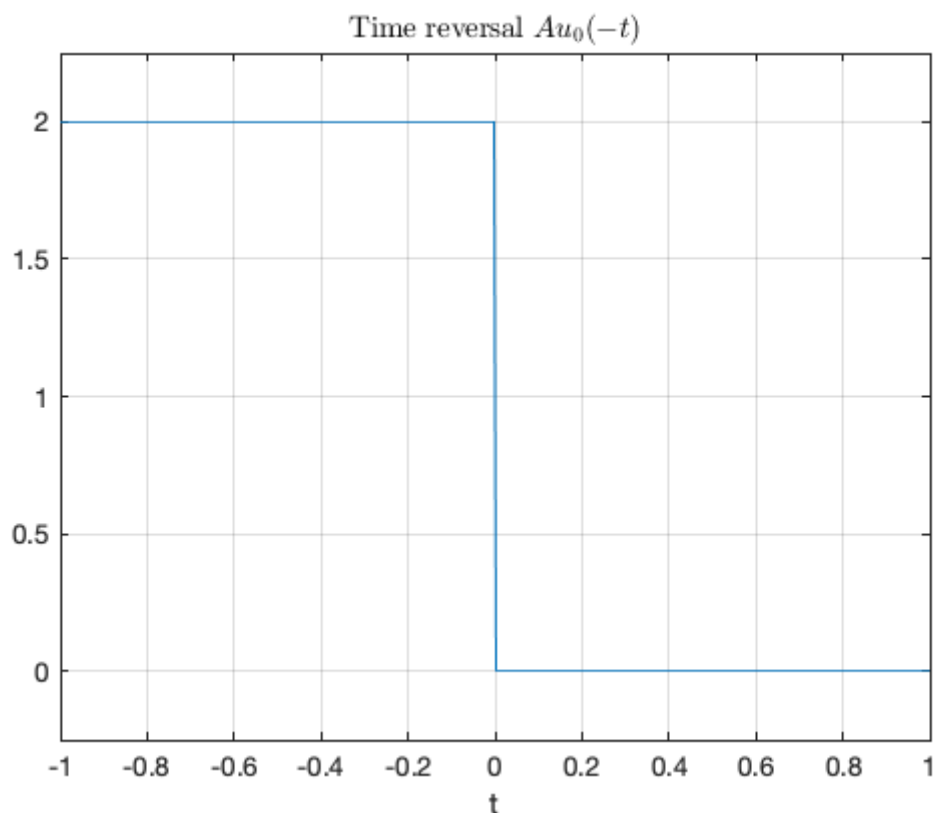
```
ezplot(A*u0(-t),[-1,1]),grid,title('Time reversal $$Au_0(-t)$$','interpreter','latex')
```




The sign on the function argument  $-t$  causes the whole signal to be reversed in time. Note that another way of looking at this is that the signal is mirrored about the  $y$  axis.

## Time Delay and Advance

Sketch  $u_0(t - T)$  and  $u_0(t + T)$

In [7]:

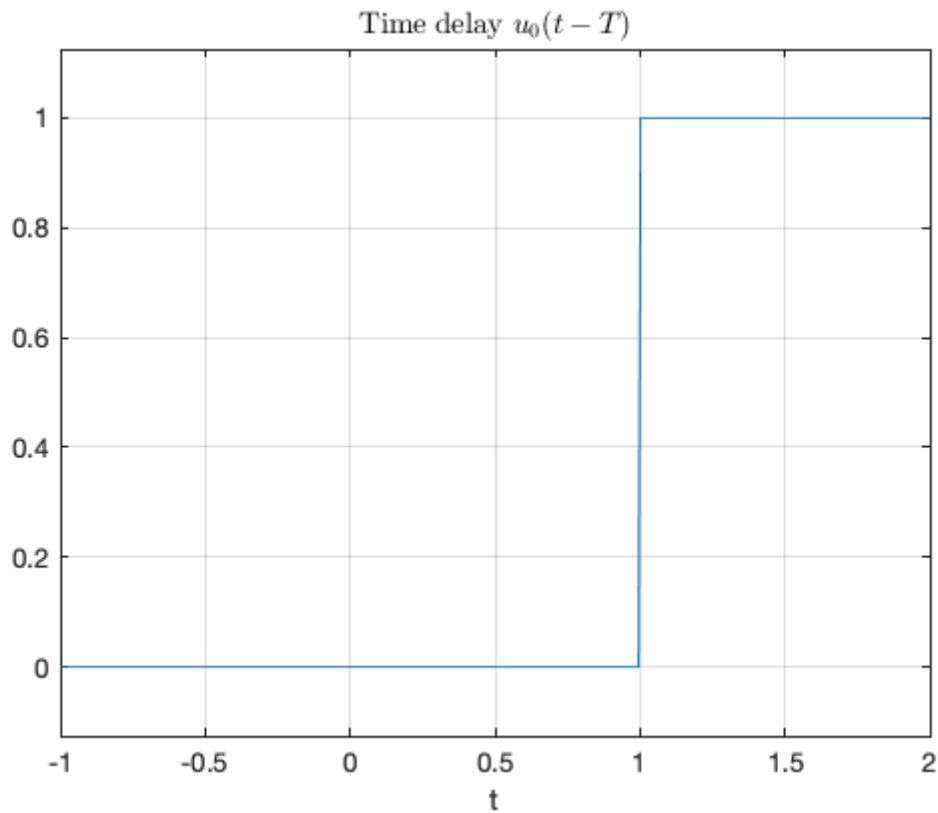
```
T = 1; % again to make the signal plottable.  
ezplot(u0(t - T),[-1,2]),grid,title('Time delay  $u_0(t - T)$ ','interpreter','l  
atex')
```



This is a *time delay* ... note for  $u_0(t - T)$  the step change occurs  $T$  seconds **later** than it does for  $u_o(t)$ .

In [8]:
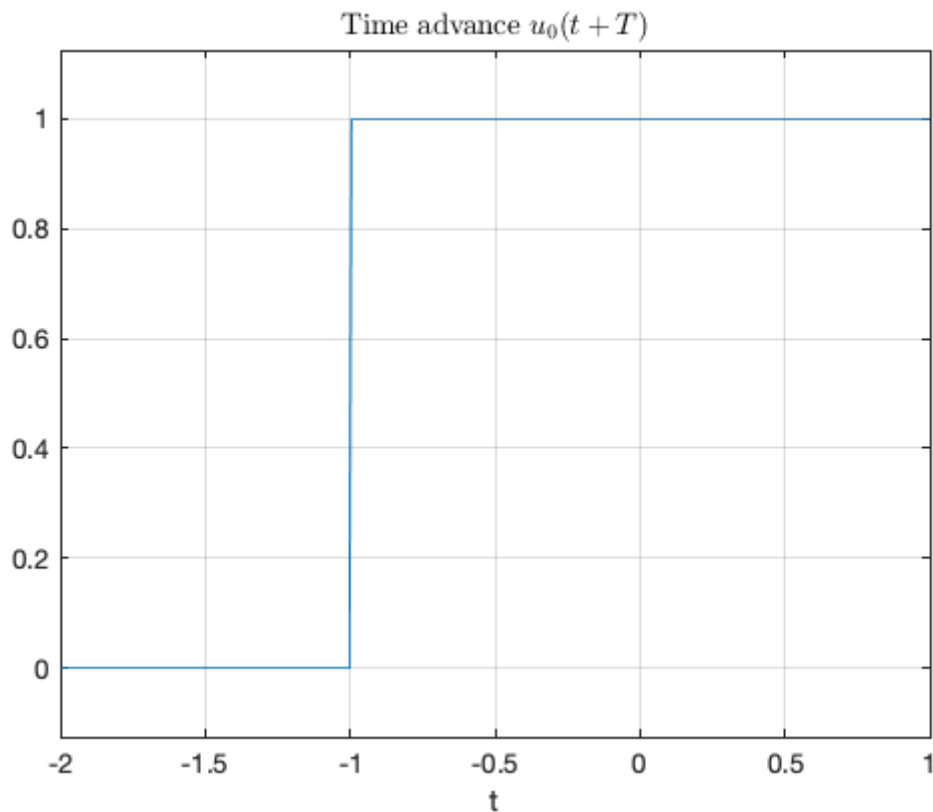
```
ezplot(u0(t + T),[-2,1]),grid,title('Time advance $$u_0(t + T)$$','interpreter',
'latex')
```



This is a *time advance* ... note for  $u_0(t + T)$  the step change occurs  $T$  seconds **earlier** than it does for  $u_0(t)$ .

## Examples


We will work through some examples in class. See [Worksheet 3 \(worksheet3\)](#).

## Synthesis of Signals from the Unit Step

Unit step functions can be used to represent other time-varying functions such as rectangular pulses, square waves and triangular pulses. See [Worksheet 3 \(worksheet3\)](#) for the examples that we will look at in class.



## The Ramp Function

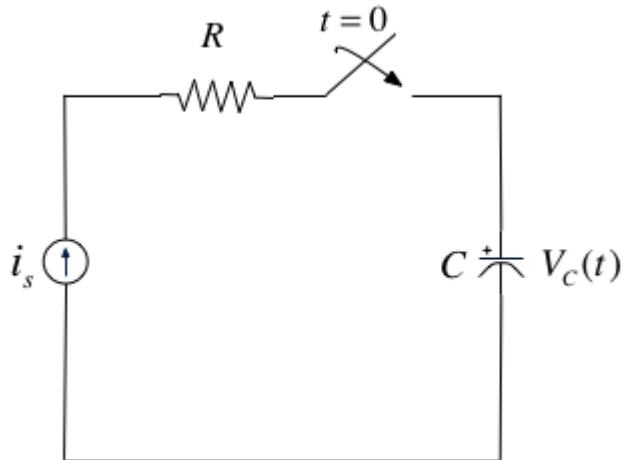

In the circuit shown above  $i_s$  is a constant current source and the switch is closed at time  $t = 0$ .

When the current through the capacitor  $i_c(t) = i_s$  is a constant and the voltage across the capacitor is

$$v_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(\tau) d\tau$$

where  $\tau$  is a dummy variable.

Since the switch closes at  $t = 0$ , we can express the current  $i_c(t)$  as

$$i_c(t) = i_s u_0(t)$$

and if  $v_c(t) = 0$  for  $t < 0$  we have

$$v_c(t) = \frac{1}{C} \int_{-\infty}^t i_s u_0(\tau) d\tau = \underbrace{\frac{i_s}{C} \int_{-\infty}^0 i_c(\tau) d\tau}_0 + \frac{i_s}{C} \int_0^t i_c(\tau) d\tau$$


So, the voltage across the capacitor can be represented as

$$v_c(t) = \frac{i_s}{C} t u_0(t)$$

To sketch the wave form, let's arbitrarily let  $C$  and  $i_s$  be one and then plot with MATLAB.

In [12]:
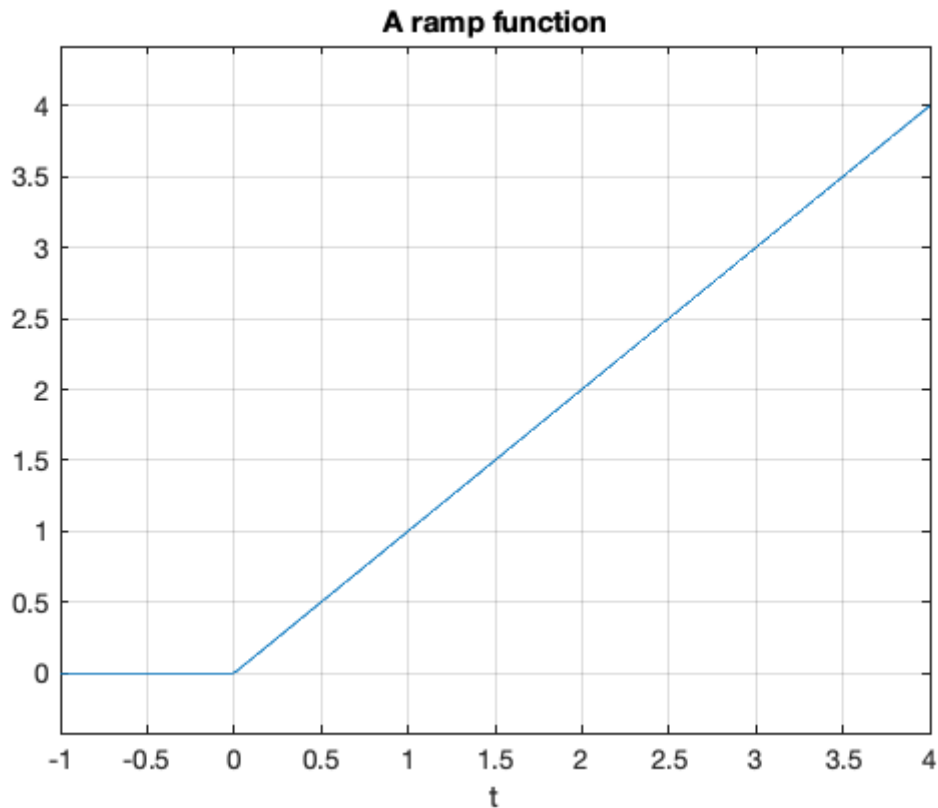
```
C = 1; is = 1;
vc(t)=(is/C)*t*u0(t);
ezplot(vc(t),[-1,4]),grid,title('A ramp function')
```



This type of signal is called a **ramp function**. Note that it is the *integral* of the step function (the resistor-capacitor circuit implements a simple integrator circuit).

The unit ramp function is defined as

$$u_1(t) = \int_{-\infty}^t u_0(\tau) d\tau$$

so

$$u_1(t) = \begin{cases} 0 & t < 0 \\ t & t \geq 0 \end{cases}$$

and

$$u_0(t) = \frac{d}{dt} u_1(t)$$

## Note


Higher order functions of  $t$  can be generated by the repeated integration of the unit step function.

For future reference, you should determine  $u_2(t)$ ,  $u_3(t)$  and  $u_n(t)$  for yourself and make a note of the general rule:

$$u_{n-1} = \frac{1}{n} \frac{d}{dt} u_n(t)$$

Details are given in equations 1.26–1.29 in Karris.

## The Dirac Delta Function

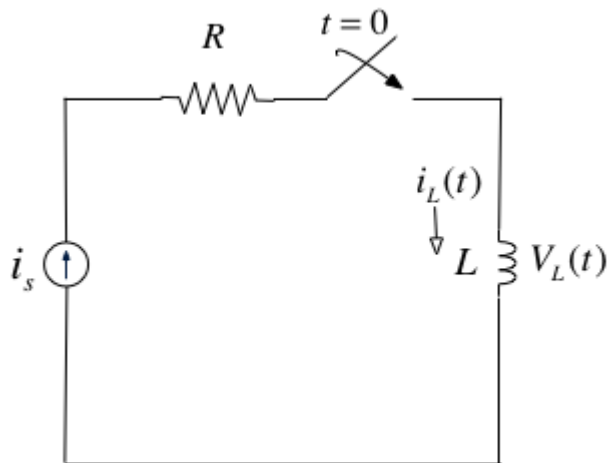

In the circuit shown above, the switch is closed at time  $t = 0$  and  $i_L(t) = 0$  for  $t < 0$ . Express the inductor current  $i_L(t)$  in terms of the unit step function and hence derive an expression for  $v_L(t)$ .

## Solution

$$v_L(t) = L \frac{di_L}{dt}$$

Because the switch closes instantaneously at  $t = 0$

$$i_L(t) = i_s u_0(t)$$

Thus

$$v_L(t) = i_s L \frac{d}{dt} u_0(t).$$

To solve this problem we need to invent a function that represents the derivative of the unit step function. This function is called  $\delta(t)$  or the *dirac delta* function (named after Paul Dirac ([http://en.wikipedia.org/wiki/Paul\\_Dirac](http://en.wikipedia.org/wiki/Paul_Dirac))).

## The delta function

The unit impulse or the delta function, denoted as  $\delta(t)$ , is the derivative of the unit step.

This function is tricky because  $u_0(t)$  is discontinuous at  $t = 0$  but it must have the properties

$$\int_{-\infty}^t \delta(\tau) d\tau = u_0(t)$$

and

$$\delta(t) = 0 \quad \forall t \neq 0.$$

## Sketch of the delta function



## MATLAB Confirmation

In [11]:

```
syms is L;
vL(t) = is * L * diff(u0(t))
```

```
vL(t) =
L*is*dirac(t)
```

Note that we can't plot `dirac(t)` in MATLAB with `ezplot`.

## Important properties of the delta function

### Sampling Property

The *sampling property* of the delta function states that

$$f(t)\delta(t-a) = f(a)\delta(t-a)$$

or, when  $a = 0$ ,

$$f(t)\delta(t) = f(0)\delta(t)$$

Multiplication of any function  $f(t)$  by the delta function  $\delta(t)$  results in sampling the function at the time instants for which the delta function is not zero.

The study of discrete-time (sampled) systems is based on this property.

*You should work through the proof for yourself.*

## Sifting Property

The *sifting property* of the delta function states that

$$\int_{-\infty}^{\infty} f(t)\delta(t - \alpha)dt = f(\alpha)$$

That is, if multiply any function  $f(t)$  by  $\delta(t - \alpha)$ , and integrate from  $-\infty$  to  $+\infty$ , we will get the value of  $f(t)$  evaluated at  $t = \alpha$ .

*You should also work through the proof for yourself.*

## Higher Order Delta Functions

the  $n$ th-order *delta function* is defined as the  $n$ th derivative of  $u_0(t)$ , that is

$$\delta^n(t) = \frac{d^n}{dt^n} [u_0(t)]$$

The function  $\delta'(t)$  is called the *doublet*,  $\delta''(t)$  is called the *triplet* and so on.

By a procedure similar to the derivation of the sampling property we can show that

$$f(t)\delta'(t - a) = f(a)\delta'(t - a) - f'(t)\delta(t - a)$$

Also, derivation of the sifting property can be extended to show that

$$\int_{-\infty}^{\infty} f(t)\delta^n(t - \alpha)dt = (-1)^n \frac{d^n}{dt^n} [f(t)] \Big|_{t=\alpha}$$

## Summary

In this chapter we have looked at some elementary signals and the theoretical circuits that can be used to generate them.

## Takeaways

- You should note that the unit step is the *heaviside function*  $u_0(t)$ .
- Many useful signals can be synthesized by use of the unit step as a "gating function" in combination with other signals
- That unit ramp function  $u_1(t)$  is the integral of the step function.
- The *Dirac delta* function  $\delta(t)$  is the derivative of the unit step function. We sometimes refer to it as the *unit impulse function*.
- The delta function has sampling and sifting properties that will be useful in the development of *time convolution* and *sampling theory*.

## Examples

We will do some of these in class. See [worksheet3 \(worksheet3\)](#).

## Homework

These are for you to do later for further practice. See [Homework 1 \(./homework/hw1\)](#).